



Sharif University of Technology
Department of Computer Engineering

Low Power Digital System Design

Circuit-Level LPD Techniques

A. Ejlali

Circuit-Level LPD Techniques

- Example of circuit-level LPD techniques:
 - Multi- V_t circuits
 - Multi- V_{DD} circuits
 - Minimizing device count and internal swing (Proper CMOS logic style).
 - Pseudo NMOS, CPL
 - Custom circuit design

Dual Threshold Circuits

- Dual threshold technique can be used to deal with the leakage problem.
- Why has leakage problem become an important concern in LPD?
 - V_{DD} reduction \Rightarrow
 - Switching Power decreases quadratically
 - Sub-threshold Leakage Power decreases linearly
 - V_{th} reduction \Rightarrow
 - Increases Sub-threshold Leakage Power exponentially


Impact of Scaling on Sub-threshold Leakage Power

$$P_{SUB} = V_{DD} \cdot \beta(1-\eta)V_T^2 \underbrace{\exp\left(\frac{V_{GS} - V_{th}}{\eta V_T}\right)}_{T1} \underbrace{[1 - \exp\left(-\frac{V_{DS}}{V_T}\right)]}_{T2}$$

where $V_T = \frac{KT}{q}$

- Assume: $V_{GS} \cong 0$, $V_{DS} \cong V_{DD}$ (Realistic assumption)
- In constant field scaling, the relative variations of term $T1$ is much greater than the relative variations of term $T2$.

Power Trends of Microprocessors

 

Impact of Threshold Voltage on Circuit Performance

$$V_{th} \uparrow \Rightarrow P_{Sub} \downarrow$$

$$V_{th} \uparrow \Rightarrow Delay \uparrow$$

$$Delay \propto \frac{C_L \cdot V_{dd}}{(V_{dd} - V_{th})^\alpha}$$

Dual Threshold Circuits

- Main Idea: Assigning a **high-threshold** voltage to some transistors in **non-critical paths**, and using **low-threshold** transistors in **critical path(s)**.
- Not all the transistors in non-critical paths can be assigned a high-threshold voltage, otherwise, the critical path may change, thereby increasing the critical delay.

Dual Threshold Circuits

- Dual-threshold voltages can be achieved by:


- Body Biasing

$$V_t = V_{t0} + \gamma[\sqrt{2\Phi_b + |V_{sb}|} - \sqrt{2\Phi_b}]$$

$$V_{sb} \uparrow \Rightarrow V_{th} \uparrow$$

- Dual- V_{th} MOSFET Process
 - Channel Doping

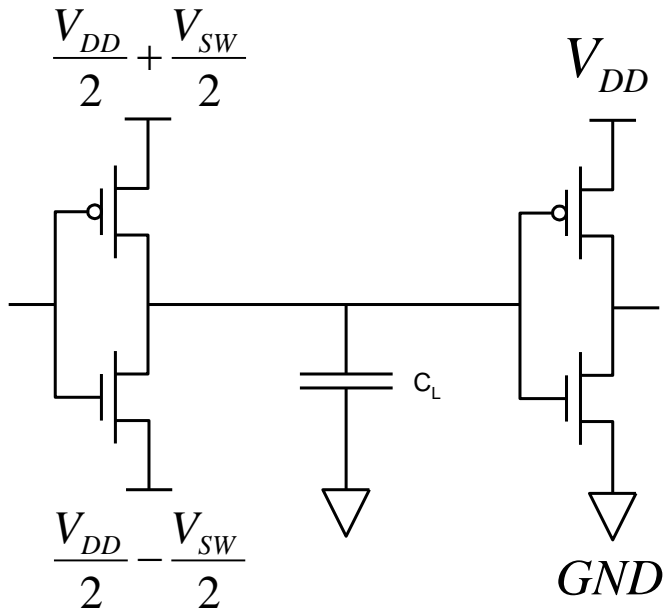Dual Threshold Circuits: Application in Level Shifters



Driver Inverter

Receiver Inverter

$$P_{SW} = \alpha \cdot f \cdot C_L \cdot V_{SW} \cdot V_{DD}$$

$$I_{REC-Static}(V_{SW}) = \begin{cases} 0 & \frac{V_{DD}}{2} - \frac{V_{SW}}{2} \leq V_{th} \\ \frac{\beta}{2} \left(\frac{V_{DD}}{2} - \frac{V_{SW}}{2} - V_{th} \right)^2 & \frac{V_{DD}}{2} - \frac{V_{SW}}{2} > V_{th} \end{cases}$$

- Assigning a **high-threshold** voltage to the transistors of the **receiver LS**, and using **low-threshold** transistors in the **driver LS**.