



Sharif University of Technology
Department of Computer Engineering

Low Power Digital System Design

Gate-Level Techniques (Cont.)

A. Ejlali

Concurrency and Redundancy

- Basic Idea: Using concurrency and redundancy to improve performance and then to **trade this performance for lower power by reducing the voltage supply**.
- This technique can be used at any level of abstraction.

Original Unit

Original Unit

Redundant Unit

$$P_{SW} = \alpha C_L V_{DD}^2 f$$

$$P'_{SW} = 2 \times \left[\alpha C_L \left(\frac{V_{DD}}{2} \right)^2 \frac{f}{2} \right] = \frac{P_{SW}}{4}$$

Impact of Supply Voltage on PDP

$$PDP = P_{SW} \times delay = \alpha C_L V_{DD}^2 f \times \frac{1}{f} = \alpha C_L V_{DD}^2$$

$$V_{DD} \downarrow \Rightarrow PDP \downarrow$$


- As V_{DD} decreases PDP decreases quadratically.
- Note that PDP can be interpreted as “Energy per Cycle” (Energy per Result).

Concurrency and Redundancy at the Gate-Level

- From a performance point of view:
 - It is **not beneficial** to improve the **speed** of the circuit part **off the critical path**.
- From a power consumption point of view:
 - It is **quite beneficial** to improve the **speed** of the circuit part **off the critical path** and then trade this speed for lower power:
(Dual V_{DD})

Concurrency and Redundancy at the Gate-Level (Cont.)

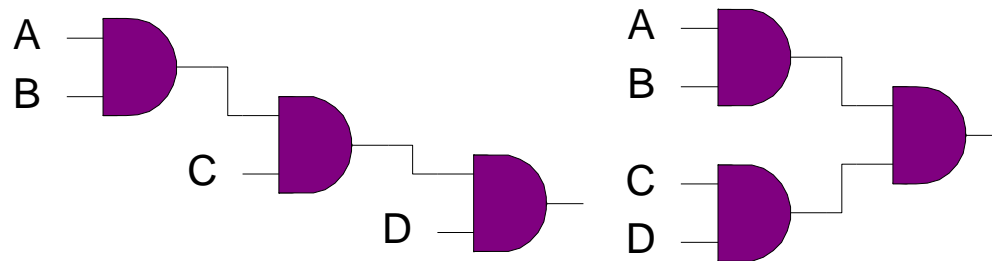- Two-step technique:
 - Reduce the circuit depth (Concurrency).
 - This can result in increased number of gates (Redundancy)
 - Apply the Dual V_{DD} technique to the circuit.
- Note: Concurrency is desirable but redundancy is not desirable. Sometimes, we can increase the concurrency without incurring any redundancy.
 - Example:




Redundancy: The Penalty for Using Concurrency

- In the concurrency and redundancy technique, redundancy usually refers to **hardware redundancy**.
 - **Area penalty**, which in turn results in an **increase in power dissipation**.
- However careful consideration must be given to **other types of penalties**.
 - Example: **increase in switching activity**.
- Solution: The concept of **effective capacitance**

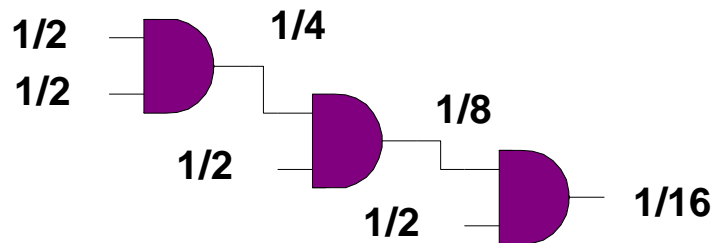
Example: Other types of penalties

- In this example, the penalty for using concurrency is not a redundant hardware, rather it is an increase in switching activity.



Switching Activity=347/256
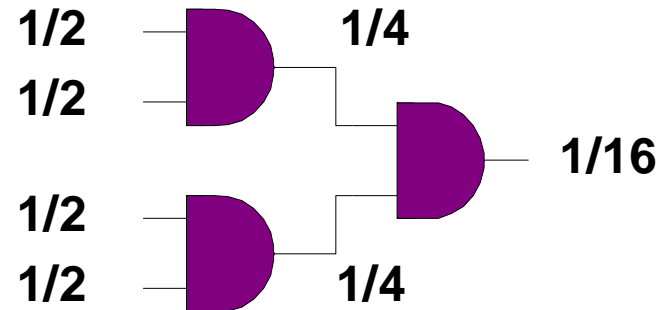
$$P_{SW} = \frac{347}{256} C_L V_{DD}^2 f$$



Switching Activity=367/256

$$P'_{SW} = \frac{367}{256} C_L \left(\frac{2}{3} V_{DD}\right)^2 \frac{2f}{3} \cong 0.31 P_{SW}$$

Effective Capacitance

- Effective capacitance represents the average capacitance switched every clock cycle.
 - Effective capacitance = Switched capacitance = C_{eff}

$$P_{SW} = C_{eff} V_{DD}^2 f \qquad C_{eff} = \alpha C_L$$

- Any increase in effective capacitance can be considered as redundancy.