



Sharif University of Technology
Department of Computer Engineering


Low Power Digital System Design

On-chip Interconnects

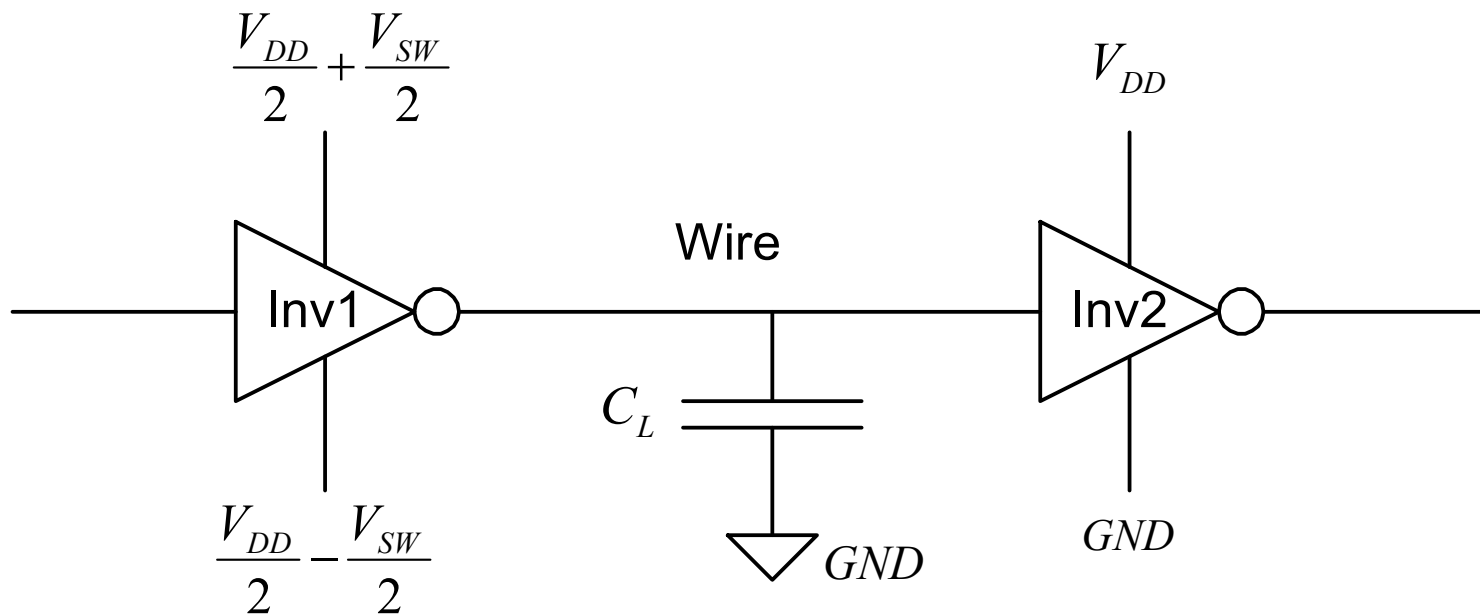
A. Ejlali

On-chip Interconnects

- Account for a significant fraction (up to 50%) of the total on-chip energy (SoC).
- One possible solution:
 - reduced voltage swing




Reduced Voltage Swing

 

$$Power \propto Amplitude^2$$

Level Shifters

- Inverters used as Level Shifters

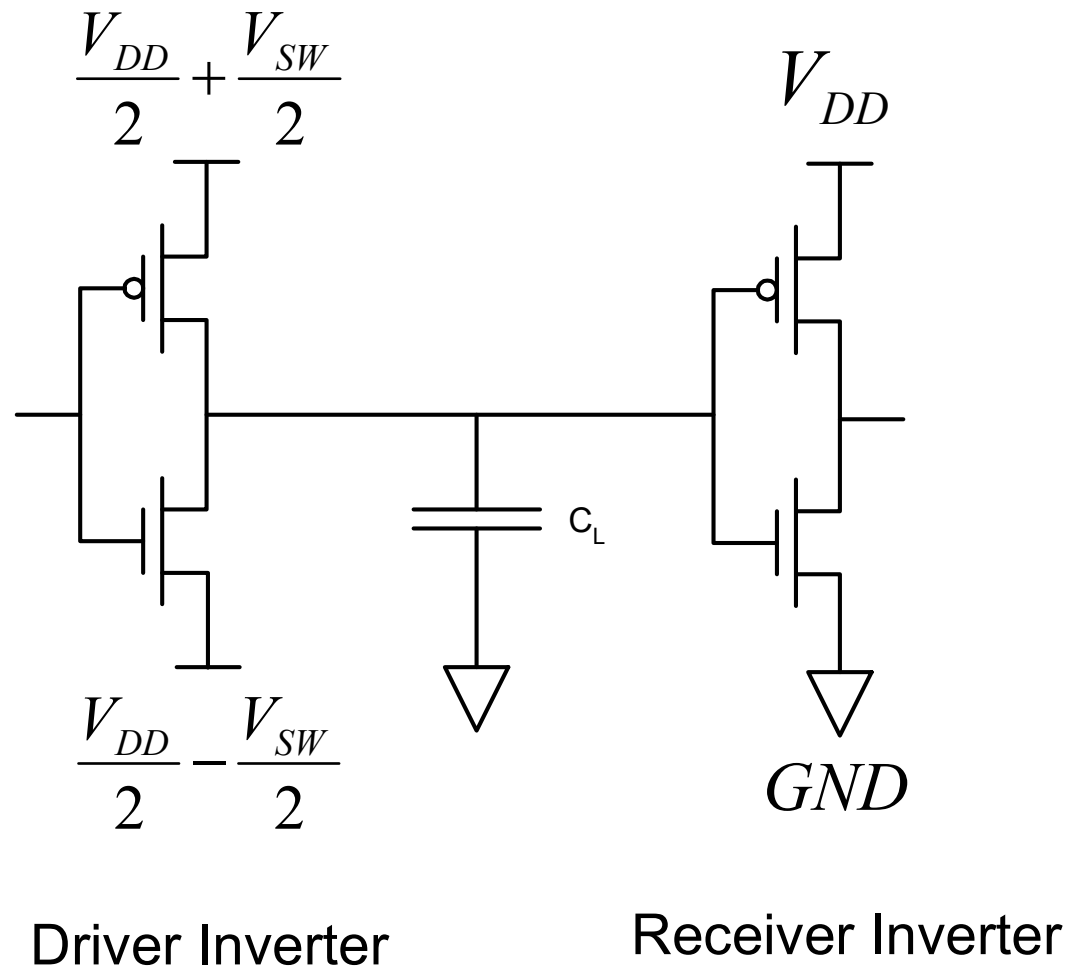

Switching Power

- Mainly consumed by driver inverter
 - Driver supply voltage is externally generated.
 - Voltage Source (efficient dc-dc converters).

$$P_{SW} = \alpha \cdot f \cdot C_L \cdot V_{SW}^2$$

- Driver supply voltage is internally generated.
- Series regulators.

$$P_{SW} = \alpha \cdot f \cdot C_L \cdot V_{SW} \cdot V_{DD}$$

Static Power

- Mainly consumed by receiver inverter
- Transistors of receiver INV may never be in sub-threshold region.

$$I_{REC-Static}(V_{SW}) = \begin{cases} 0 & \frac{V_{DD}}{2} - \frac{V_{SW}}{2} \leq V_{th} \\ \frac{\beta}{2} \left(\frac{V_{DD}}{2} - \frac{V_{SW}}{2} - V_{th} \right)^2 & \frac{V_{DD}}{2} - \frac{V_{SW}}{2} > V_{th} \end{cases}$$

Optimum Voltage Swing

$$V_{SW} \downarrow \Rightarrow P_{SW} \downarrow$$

$$V_{SW} \downarrow \Rightarrow P_{Static} \uparrow$$

- Optimum voltage swing minimizes the total power.
- It is a function of activity:

$$\alpha \downarrow \Rightarrow V_{SW} \uparrow$$

Compromising Other Objectives

- Performance (Operational Frequency):

$$f(V_{SW}) = \frac{\beta}{2C_L} \cdot \frac{(V_{SW} - V_{th})^2}{V_{SW}}$$

- Reliability (Bit Error Rate):
 - Gaussian Noise Assumption

$$BER(V_{SW}) = Q\left(\frac{V_{SW}}{2\sigma_N}\right)$$

where

$$Q(x) = \frac{1}{\sqrt{2\pi}} \int_x^{\infty} e^{-\frac{u^2}{2}} du$$

Assignment

- Analyze the power of a case-study interconnect
 - Technology: 90nm PTM
 - $C_L=0.5\text{pf}$ (Wire length=almost 2mm)
 - Aspect ratio (W/L): N:3, P:6
 - $V_{DD}=1.1\text{V}$
 - $V_{SW}=0.2\text{V}, 0.4\text{V}, 0.8\text{V}, 1\text{V}$
 - Power consumption=?
 - Cut-off frequency=?

References

Christer Svensson, "**Optimum Voltage Swing on On-Chip and Off-Chip Interconnect**", *IEEE Journal of Solid-State Circuits*, 2001.

F. Worm, *et al.* "**A Robust Self-Calibrating Transmission Scheme for On-Chip Networks**", *IEEE Transactions on VLSI*, 2005.

A. Ejlali, *et al.* "**Performability/Energy Tradeoff in Error-Control Schemes for On-Chip Networks**", *IEEE Transactions on VLSI*, 2010.