



Sharif University of Technology
Department of Computer Engineering

Low Power Digital System Design

Gate-Level Techniques

A. Ejlali



Gate-Level LPD Techniques

- Technology Decomposition and Mapping
- Activity Postponement
- Glitch Reduction
- Concurrency and Redundancy

Technology Decomposition and Mapping



- Realization of Boolean Functions
 - Switch-Level: Results in **complex** CMOS gates
 - Gate-Level: Results in networks of **simple** CMOS gates
- Example:

$$f(a,b,c) = \overline{a + bc}$$

  

Technology Decomposition and Mapping

  
- Main Idea: hide **high activity** nodes **inside** complex CMOS gates.
- Example:



d is hidden inside a complex gate

Technology Decomposition and Mapping

 - Rapidly switching signals are mapped to the **low capacitance internal nodes**.
- Example:



Technology Decomposition and Mapping

Impact on Performance

- Making a gate too complex **can** slow the circuit, resulting in a trade-off of performance for power.
 - **Stacked transistors** in the gates with large C_L
 - Decreased concurrency
- Solution: Be careful of the circuit critical path.

Estimation of Transition Probabilities

- Analytical Techniques
 - Certain kinds of input distributions
 - Re-convergent Fan-out Problem
- Circuit Simulation
 - Time-consuming
 - Realistic input stimulus

Calculation of Probabilities









- Zero delay model (ignore glitching)
- Primary inputs are uncorrelated
- Present input value is independent of the previous value

$$P(W_{0 \rightarrow 1}) = P(W_{1 \rightarrow 0}) = P(W_0) \cdot P(W_1)$$


- Note:
 - This equation is independent of circuit topology (re-convergent fan-outs).
 - The above equation is valid for static CMOS style. For dynamic CMOS style we can write:

$$P(W_{0 \rightarrow 1}) = P(W_1)$$

Output activities for static and dynamic CMOS styles

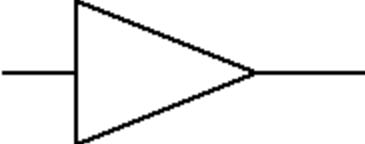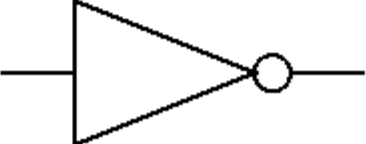$P_{out}(0 \rightarrow 1)$			$P_{out}(0 \rightarrow 1)$		
	<u>Static</u>	<u>Dynamic</u>		<u>Static</u>	<u>Dynamic</u>
	3/16	1/4		3/16	1/4
	3/16	1/4		3/16	1/4
	1/4	1/2		1/4	1/2
	1/4	1/2		1/4	1/2

Example: FA Unit (Static CMOS)

 


- Hint: The signal activity can be easily obtained from its truth table.

Probability Propagation

	$P_{0 \rightarrow 1}$
AND	$(1 - P_A P_B) P_A P_B$
OR	$(1 - P_A)(1 - P_B)(1 - (1 - P_A)(1 - P_B))$
EXOR	$(1 - (P_A + P_B - 2P_A P_B))(P_A + P_B - 2P_A P_B)$

- Assumption: Independence of input probabilities.
- Main Problem: Re-convergent Fan-outs cause cross-correlation between the inputs of a gate.

Re-convergent Fan-out

 

$$P(C=1)=P(A=1).P(B=1 | A=1)=P(B=1).P(A=1 | B=1)$$

Note: The truth table technique is still applicable