



Sharif University of Technology  
Department of Computer Engineering

# Low Power Digital System Design

Concurrency and redundancy at RT-level

A. Ejlali


# Assignment

- Develop the gate level models of:
  - Ripple carry adder
  - CLA adder
  - Hint: Develop behavioral models and use synthesis tools to generate gate-level models.
- Estimate the  $C_{eff}$  redundancy
  - Hint: Use Modelsim and use transition\*fan-out as a gate-level measure for  $C_{eff}$ , or use Synopsys power compiler.
- Estimate the speed-up of the CLA adder over the ripple carry adder.
- Estimate the power reduction factor.
  - Hint: Recall

$$P'_{SW} = (R \times C_{eff}) \cdot \left( \frac{V_{DD}}{S} \right)^2 \frac{f}{S} = \frac{R}{S^3} P_{SW}$$


# Voltage Reduction Using Parallelism

- Redundancy and concurrency

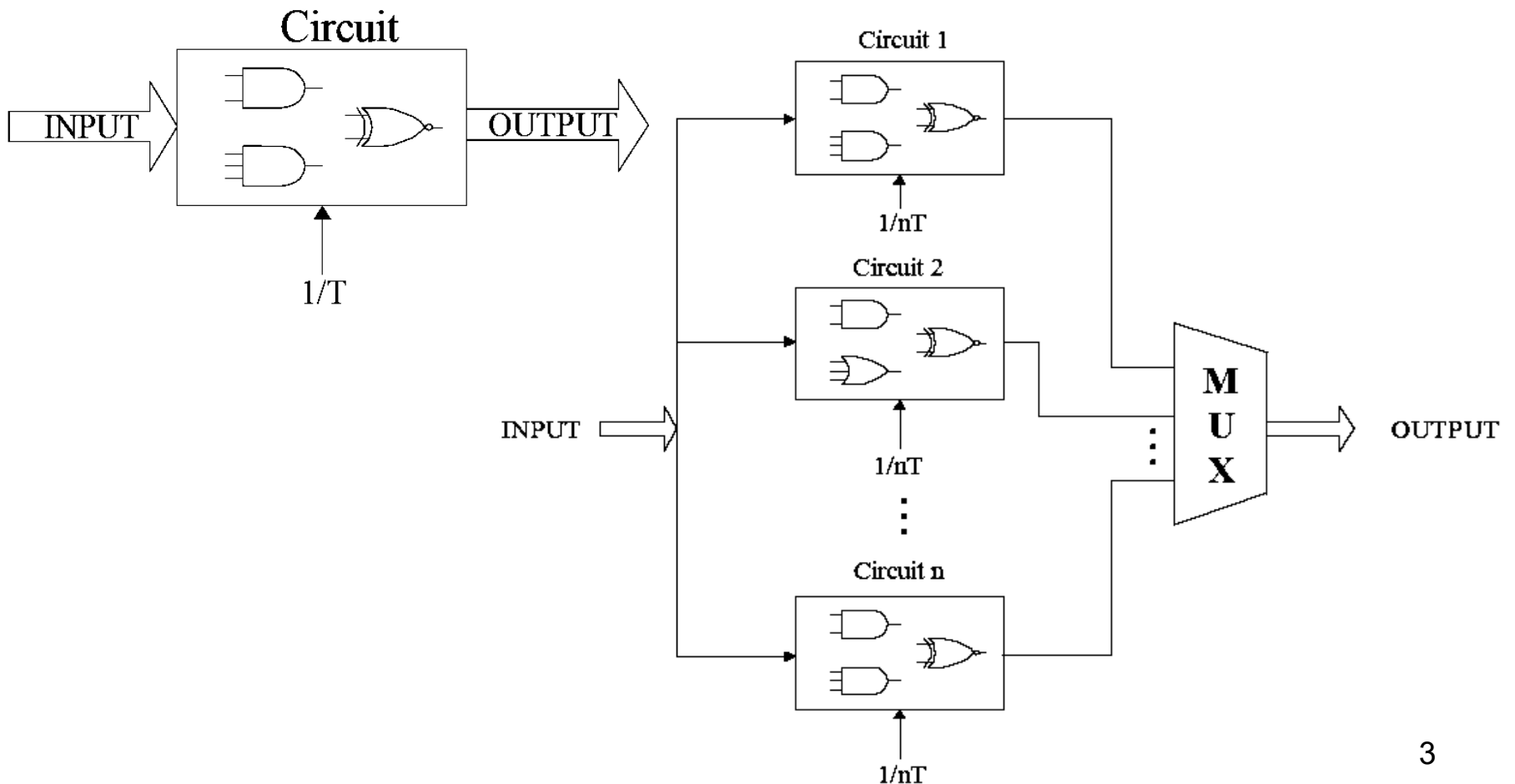





# Parallel Shift Register

- Redundancy and concurrency

 

# DFF Parallelization

- Redundancy and concurrency

    

# References

H. Mizas, et.al., "Structure of the Low-Power Design Flow", *LPGD/WP1/DUTH/ D1.2R1*, 1998.

R. Hossain, et. al., "Low Power Design Using Double Edge Triggered Flip-Flops", *IEEE Transactions on VLSI*, 1994.